 


SPED

shortest path evaluation device

Shortest Path Problem

- Given a network of nodes, find the shortest distance from A to all other nodes



Assumptions:

- weights range from 1 to 7
- up to 4 connections per node

Dijkstra's Algorithm

$T = \{A\}$

for all vertices

if v is adjacent to A

$D(v) = w(A, v)$

else $D(v) = \infty$

$T =$ termination set

$D(v) =$ current shortest
distance to v

$w(i,j) =$ weight of edge
connecting i and j

Find u not in T such that $D(u)$ is a minimum


Add u to T

for v not in T and v adjacent to u


$D(v) = \min[D(v), D(u) + w(u,v)]$

* update $D(v)$ if the path to v via u is shorter than the previous shortest path.

High Level Block Diagram

 


Simplified Data Flow

 

Network Memory

- 8 rows each consisting of 19 bits of storage
- Each row containing all information for one vertex
- First 7 bits storing connections
- Last 12 bits storing weights

Network Memory – Buffer/Latch

 

Total Weight Memory


Function : Stores the current shortest distance $D(v)$ for each vertex.

Problem : Cell takes in four 6-bit buses simultaneously and must be able to read and store to any combination of the seven columns.

Solution :


- Array of T-gates
- Four 3 to 8 decoders
- Translation PLA

Total Weight Memory

 


Add/Compare

 - Chip's main logic unit
- Under General PLA's control




Determining Next Vertex

 - 2 to 6-way comparison
 - Takes advantage of rarity of having many active nodes
 - Run by Go PLA




Two Phase Timing

 


General PLA

 - Compares weights of newly discovered paths to current path
- Updates with new path if shorter




GO PLA

 - Finds the next current vertex.
- Performs up to a 6 way comparison using the four 6-bit adders.




Critical Path

 - 6 bit ripple carry adder in add compare unit
- Longest delay ~ 8.4 ns
- Estimated clock frequency ~ 30 MHz



Chip Layout

 

Conclusion

- Design Challenges

Parallel operation – need to read out and operate on 4 sets of values

- Applicability

Computer Network – shortest path in which to transfer data

- Scalable

Easily handles increase in problem complexity