



ENGI 128



INTRODUCTION TO ENGINEERING SYSTEMS

Lecture 5: Voltage Dividers and Non-Linear Elements: LEDs

“Understand Your Technical World”


Schematics

Schematic Symbols

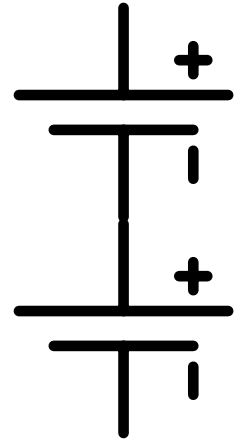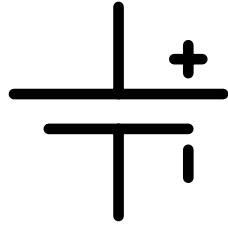

A Schematic Diagram: The Voltage Divider

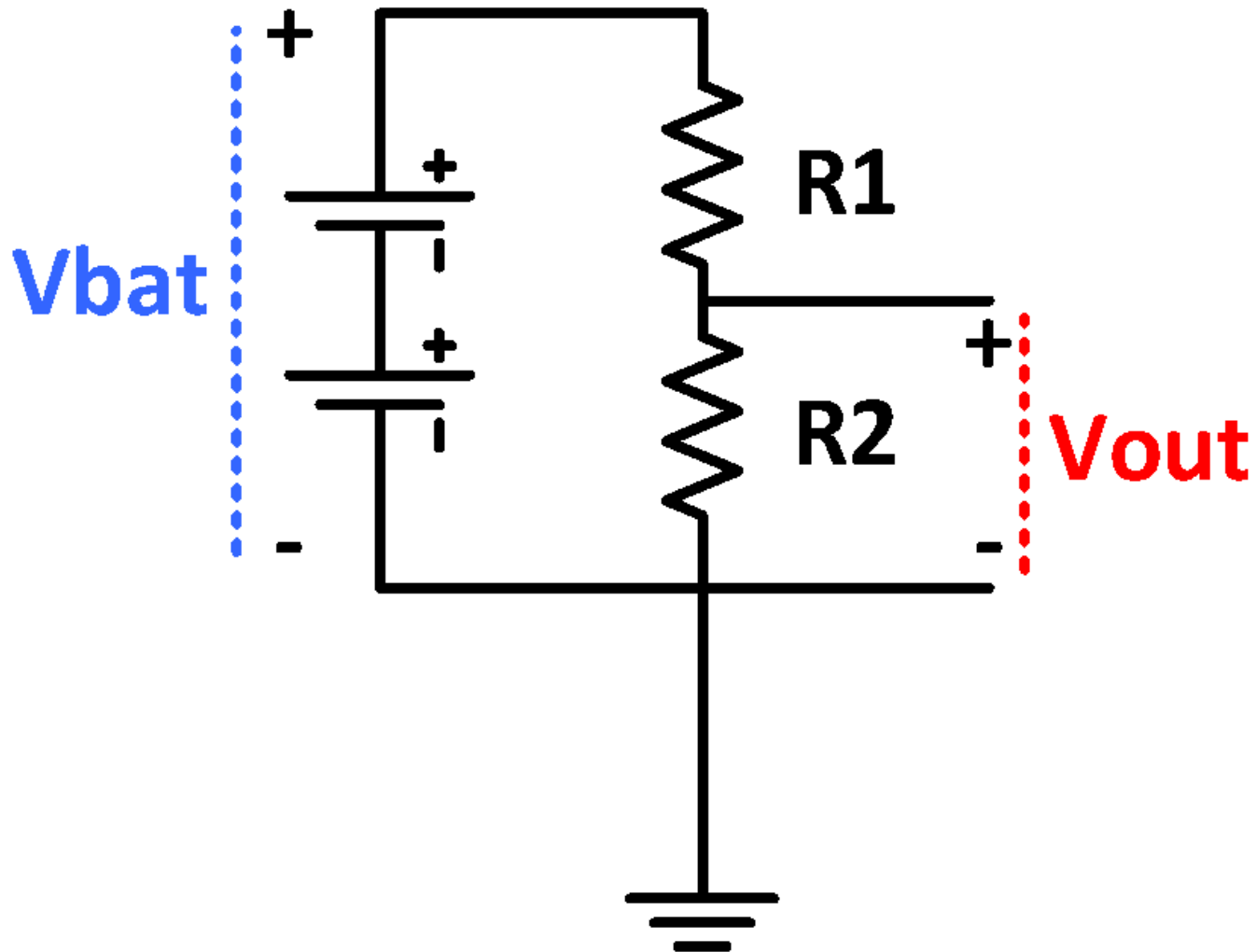Single most useful circuit on the planet:



The Voltage Divider

Voltage Divider Math

Ohm's Law


$$\begin{aligned} v &= i r \\ v_{R1} &= i_{R1} \cdot R1 \\ v_{R2} &= i_{R2} \cdot R2 \end{aligned}$$

Conservation of current

$$i_{R1} = i_{R2} = i_{bat} = i$$

Kirchhoff's voltage law
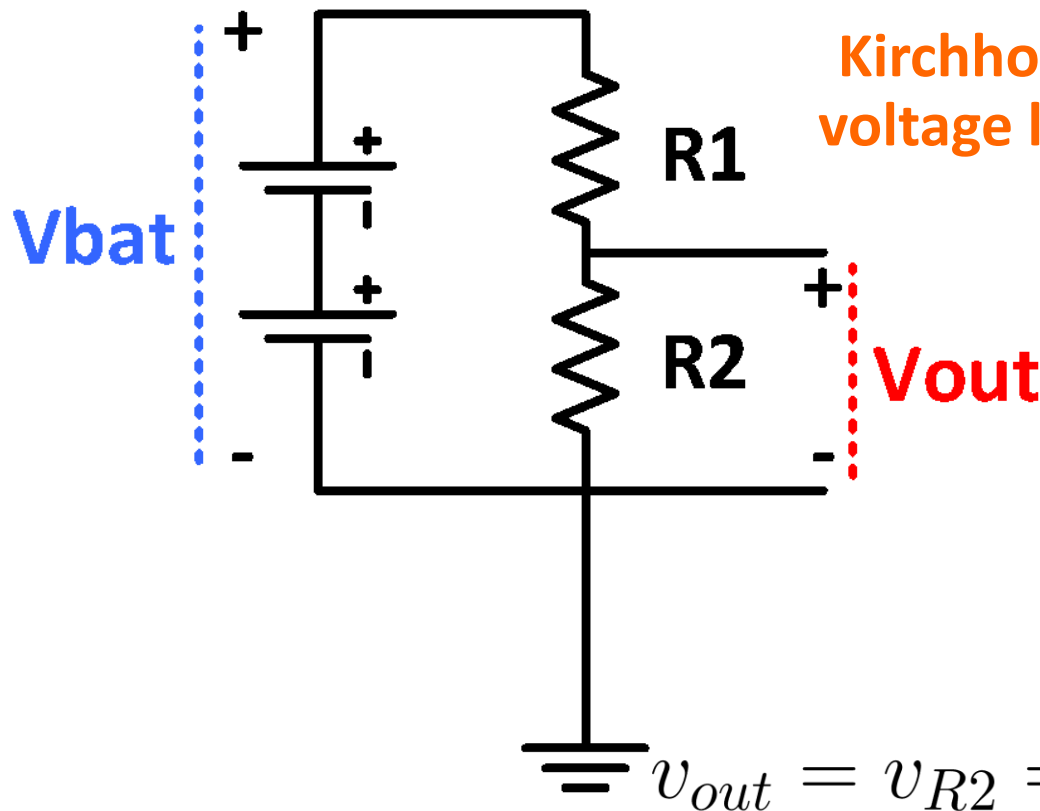
$$\begin{aligned} v_{out} &= v_{R2} \\ v_{bat} &= v_{R1} + v_{R2} \end{aligned}$$



$$v_{bat} = i \cdot R1 + i \cdot R2$$

$$v_{bat} = i(R1 + R2)$$

$$i = \frac{v_{bat}}{R1 + R2}$$

$$v_{out} = v_{R2} = i \cdot R2 = v_{bat} \frac{R2}{R1 + R2}$$

Non-Linear Elements

Non-What?

What does “non-linear” mean?

Why does it make our lives difficult?

The Humble LED

LED = Light-Emitting Diode


- They are used everywhere, in almost everything.

Wait, what's a Diode?



The Diode

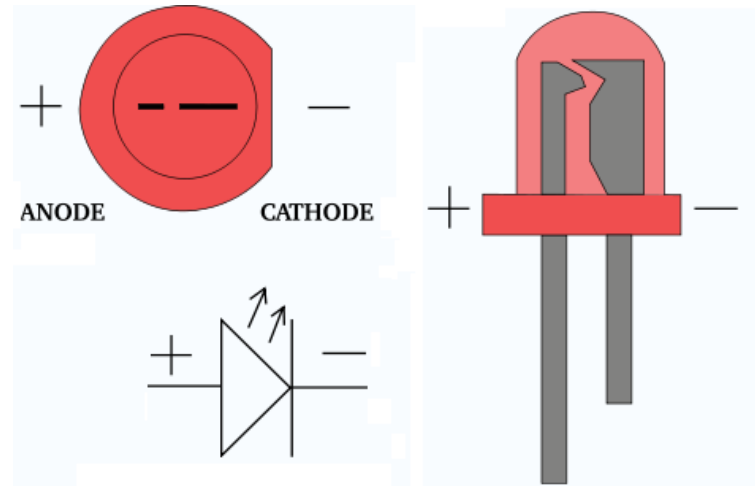
A diode only lets current flow in one direction



Ok, so what makes a LED non-linear?



$$i = \frac{v}{r}$$

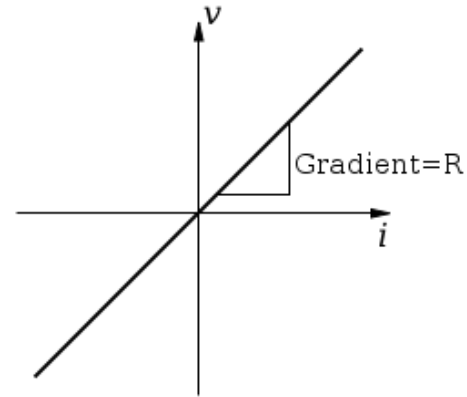


$$i = i_s(e^{V_D/(nV_T)} - 1), V_T = \frac{kT}{q}$$

oh...

The Diode Equation


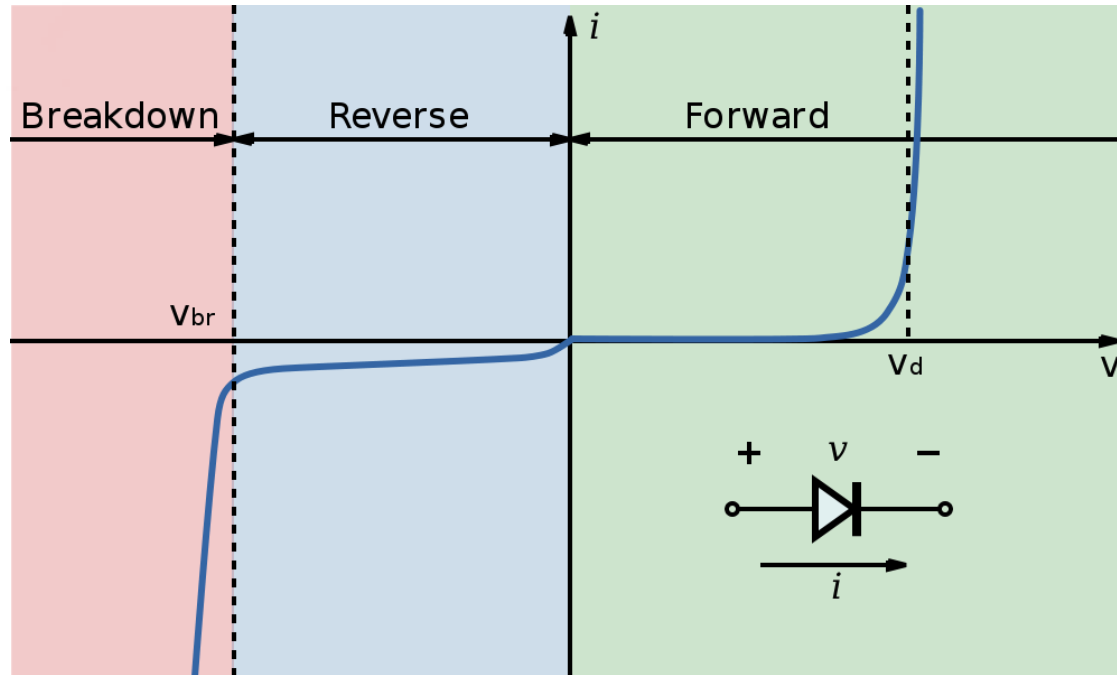
$$i = i_s \left(e^{V_D / (nV_T)} - 1 \right), V_T = \frac{kT}{q}$$



If $V_d = 0.8\text{V}$, how much current flows for a voltage of 3.3V ?


This looks complicated...

Working with Non-Linear Elements, Part I

How can we get a grip on this equation in a circuit?

- Simplify the non-linearity:

The Simplified Diode Model

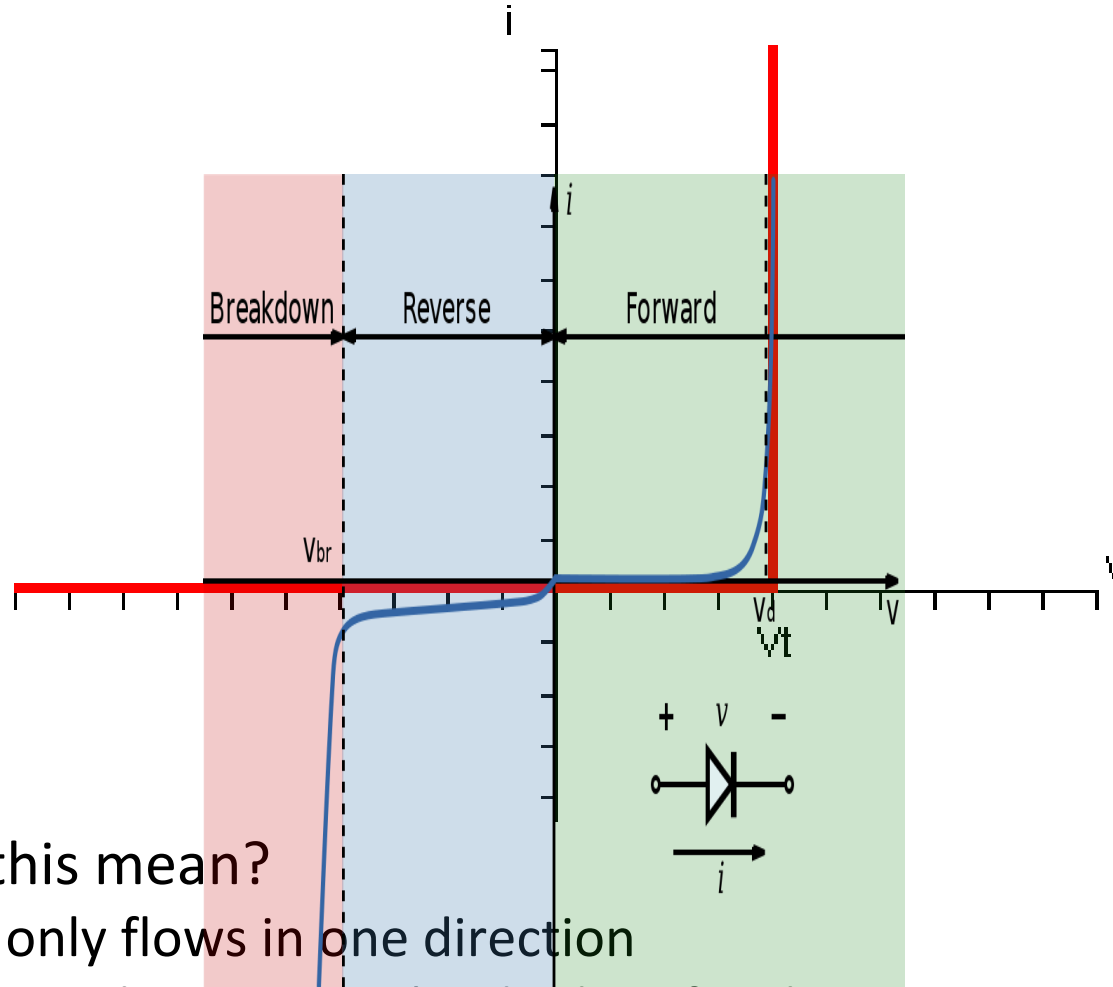

What does this mean?

- Current only flows in one direction
- The voltage drop across the diode is fixed!
- We lose V_t volts across the diode, no matter how much current flows

If $V_t = 0.8\text{v}$, how much current flows for a voltage of 1.0v or 3.3v ?

Working with Non-Linear Elements, Part II

How can we get a grip on this equation in a circuit?

- Simplify the non-linearity
- We will use the fixed voltage drop

Use a linear element to cope with this non-linear element

- A resistor can be a current limiter?

[whiteboard]

Now, how much current flows for a voltage of 3.3v?


Ta-da! Sanity.

Lab 02: Building Circuits on Breadboards

Solderless Breadboard

This lets you build circuits quickly

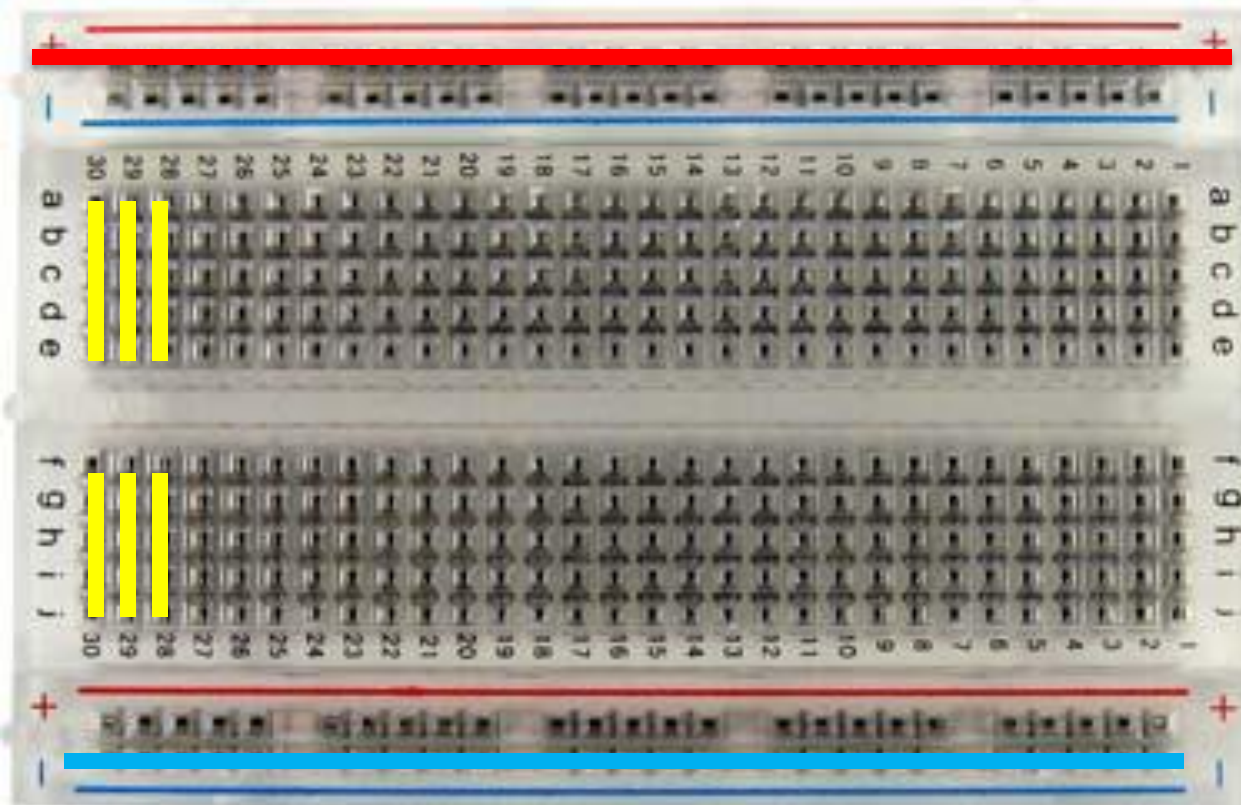- The long rows are connected horizontally
- The short columns are connected vertically




The Multimeter



OK, all together now:

- Measuring voltage
- Measuring resistance

reading resistors: color codes

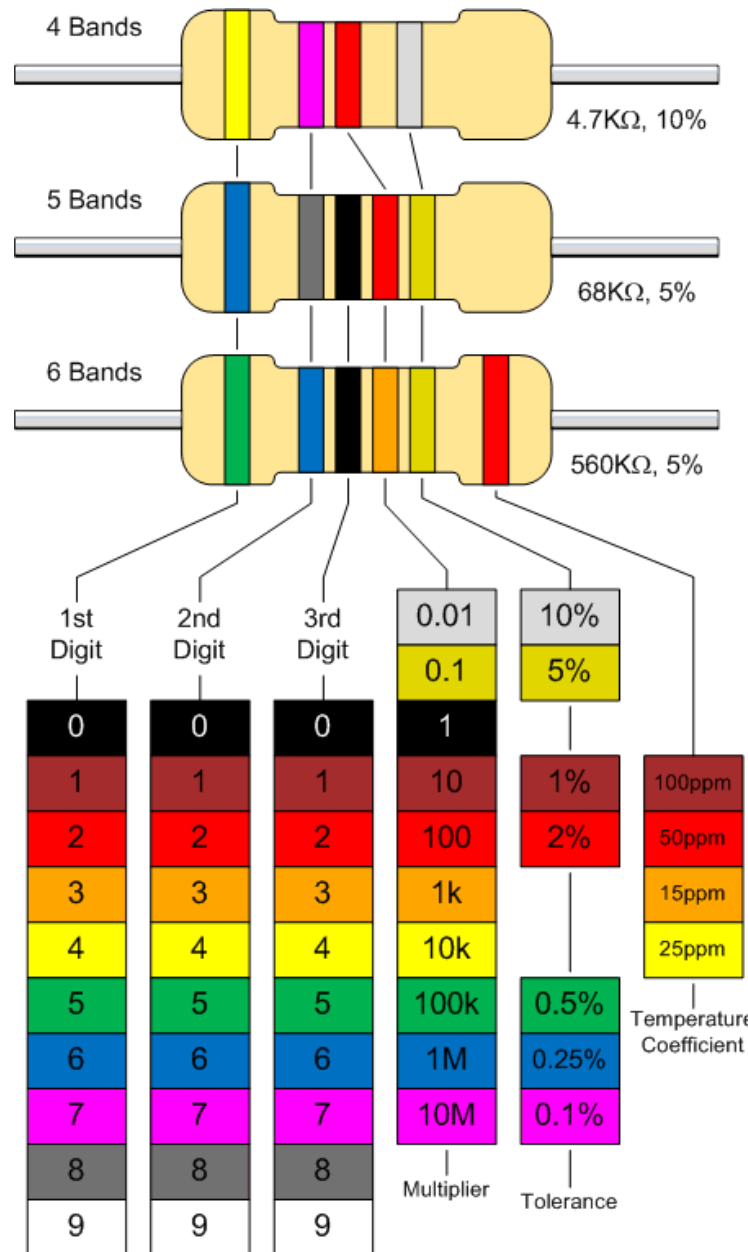

Books

Getting Started in Electronics

Make Magazine

